

# Ohm's Law



Ohm's Law describes the proportional relationship between the current flowing through a circuit and the potential difference between two points. The formula,  $V = IR$ , where  $I$  = current in amps,  $V$  = potential difference in volts, and  $R$  = resistance in ohms, details the ratio between a constant resistance and the effect of current on the voltage output. This relationship forms the basis for many electrical circuits and helps to describe the interaction between components.

**Requirements** (Check when complete):

***This section focuses on developing an understanding of the base principles governing Ohm's Law***

Do EACH of the following and submit to your instructor:

- Identify and describe the effect of current( $I$ ) on Ohm's Law, calculate for  $I$
- Identify and describe the effect of resistance( $R$ ) on Ohm's Law, calculate for  $R$
- Identify and describe the effect of voltage( $V$ ) on Ohm's Law, calculate for  $V$

***This section focuses on measurements that help to explain Ohm's Law's principles***

Do EACH of the following and submit to your instructor:

- Using a pencil and blank sheet of paper, produce three lines of varying lengths
  - Make sure that a good amount of graphite is deposited onto the paper
- Configure your power supply to output 5V DC
- Connect your power supply leads to the corresponding leads of your multimeter
- Carefully touch the negative lead to one side of your graphite line and the positive lead to the other. Record the resistance
- Calculate the current flowing through the circuit
- Adjust the position of the positive lead closer to the negative lead. Record the resistance
- Calculate the new current flowing through the circuit
- Identify and describe the effect of resistance on current in your pencil lead experiment. Repeat for the other two lines.

Do EACH of the following and submit to your instructor:

- Configure and use your multimeter to measure DC voltage
- Configure your power supply to output 5V DC
- Construct a simple breadboard circuit that connects the power supplied anode and cathode through a 1KOhm resistor.
- Use your multimeter to measure the voltage across the resistor and record the result
- Calculate the current flowing through the resistor
- Configure your multimeter to measure current
- Attach your multimeter in series with your resistor and record the current flowing through the circuit
- Calculate the value of the resistor based on your current measurement
- Calculate the voltage of your power supply using your calculated current and resistance

# Ohm's Law

***This section focuses on demonstrating Ohm's Law through a physical application***

Do ONE of the following and submit to your instructor:

- Design a simple circuit that uses a 10KOhm potentiometer instead of a fixed resistor. Connect your potentiometer as before, and limit your power supply current to 100mA. Record the effect of resistance on the circuit.
- Determine the voltage drop over a copper conductor. Describe the relationship between conductor thickness, temperature and resistance.
- Construct a simple LED dropping resistor circuit. Use Ohm's Law to determine the current draw and internal resistance of your LED.